5-stage Pipelined Processor Design Report

Team #4

Mohamed Shawky SEC:2, BN:16

Remonda Talaat SEC:1, BN:20

Evram Youssef SEC:1, BN:9

Mahmoud Adas SEC:2, BN:21

March 30, 2020

Contents

Ι	Int	roduction	1
	0.1	System Overview	2
	0.2	Task Distribution	2
II	O	verall System	3
	0.3	Overall System Design Schema	4
	0.4	Memory Specs	4
	0.5	PC Control Unit	4
		0.5.1 Inputs	4
		0.5.2 Outputs	5
		0.5.3 Logic	5
	0.6	Dynamic Branch Prediction	5
	0.7	Branch Address Unit	5
		0.7.1 Inputs	5
		0.7.2 Outputs	5
		0.7.3 Logic	6
	0.8	Register File	6
		0.8.1 Registers	6
		0.8.2 Inputs	7
		0.8.3 Outputs	7
		0.8.4 Logic	7
	0.9	ALU	7
II	ΙΙ	nstruction Format	8
	0.10	One Operand Operations	9
		Special Operations	9
	0.12	Two Operand Operations	9

	0.13 Memory Operation 0.14 Branch and Chang							
I	IV Control Signal	\mathbf{s}						12
\mathbf{V}	V Pipeline Stages							14
	0.15 Overview					 	 	 15
	$0.16~\mathrm{IF/ID~Buffer}$							
	0.17 ID/EX Buffer							
	$0.18~{ m EX/M~Buffer}$							
	$0.19~\mathrm{M/WB~Buffer}$							
\mathbf{V}	VI Pipeline Hazar	ds and s	olut	ions	5			16
	0.20 Hazards Detection	and Handl	ing .			 	 	 17
	0.20.1 Structural							
	0.20.2 Data Haza							
	0.20.3 Control Ha							

List of Figures

1	Overall System Design												4
2	Register File Diagram												6

List of Tables

1	One Operand Instruction Mapping								Ĝ
2	Two Operand Instruction Mapping								10
3	Memory Instruction Mapping								11
4	One Operand Instruction Mapping								11

Part I Introduction

0.1 System Overview

This document reports our design work of the 5-stage pipelined processor using Harvard architecture. We discuss the overall system blocks and connections, the functionalities of the different blocks and the hazard solutions.

0.2 Task Distribution

TODO: Task distribution table

Part II Overall System

South Signal Forested Nature Forested Nature Forested States Forested Nature Forested States Forested States Forested Nature Forested States Forested

0.3 Overall System Design Schema

Figure 1: Overall System Design

TODO(1): Add branch predictor design

TODO(2): Add Interrupt handling design

TODO(3): Add stack pointer related instructions design

0.4 Memory Specs

TODO: Add both memory specs and figures

0.5 PC Control Unit

0.5.1 Inputs

• IF Flush (1 bit)

- Stall Signal (1 bit)
- RESET Signal (1 bit)

0.5.2 Outputs

• PC Mux Selectors (2 bits)

0.5.3 Logic

- If IF Flush == 1, Output = 01
- If RESET == 1, Output = 10
- If Stall == 1, Output = 11
- Else, Output = 00

0.6 Dynamic Branch Prediction

TODO: Add branch prediction details in both overall diagram and section

0.7 Branch Address Unit

0.7.1 Inputs

- PC Next Address (32 bits)
- Instruction Address (32 bits)
- OpCode (7 bits)

0.7.2 Outputs

- IF Flush (1 bit)
- Branch Address (32 bits)

0.7.3 Logic

- Check if OpCode is of a branch instruction, if true:
 - Check whether PC Next Address is equal to Instruction Address
 - If true:
 - * IF Flush = 0, Branch Address = Instruction Address
 - If false:
 - * IF Flush = 1, Branch Address = Instruction Address

0.8 Register File

 


Figure 2: Register File Diagram

0.8.1 Registers

• 8 general purpose registers

- Stack pointer (SP) register
- Program counter (PC) register

0.8.2 Inputs

- Dest Regs: 2X4 bits (for destination selection)
- SRC Regs: 2X4 bits (for source selection)
- WB values: 2X32 bits (for write back values)
- RESET: 1 bit (for registers clear).
- Branch/IO: 2 bits (to determine whether the operation is IO or branch)
- IN Port: 32 bits (IO input port)

0.8.3 Outputs

- OP1: 32 bits (value of first operand)
- OP2: 32 bits (value of second operand)
- Instruction Address: 32 bits (value of branch address)
- OUT Port: 32 bits (IO output port)

0.8.4 Logic

The register selector acts like a decoder to select the required operation and the register on which the operation performed.

0.9 ALU

TODO: Add ALU flow

Part III Instruction Format

0.10 One Operand Operations

- 4 bits (1111) for one operand instructions.
- 3 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- Total of 11 bits, padded with 5 0's to fit 16 bits.

Table 1. One Operand Instruction Mapping										
Operation	OpCode	Destination	16 32	Conditions						
IN	1111000	000:111	0							
NOT	1111001	000:111	0	if $!Rdst=0,Z=1$						
				if $!Rdst<0,N=1$						
INC	1111010	000:111	0	if Rdst+1=0,Z=1						
				if $Rdst+1<0,N=1$						
DEC	1111011	000:111	0	if Rdst-1=0,Z=1						
				if Rdst-1<0,N=1						
OUT	1111100	000:111	0							

Table 1: One Operand Instruction Mapping

0.11 Special Operations

• 16 0's to represent NOP (0000000000000000).

0.12 Two Operand Operations

- 4 bits to define instruction.
- 3 bits for each of Rsrc1, Rsrc2 and Rdst.
- 1 bit to define the memory slots occupied by the instruction.
- 16 bits for immediate values.
- Total of 14 bits in most cases with some exceptions mentioned below.

Operation	OpCode	Rsrc1	Rsrc2	Rdst	dst imm		Conditions
SWAP	0001	000:111		000:111	_	0	
							_
ADD	0010	000:111	000:111	000:111		0	if Result=0,Z=1
							if Result<0,N=1
SUB	0011	000:111	000:111	000:111		0	if Result=0,Z=1
							if Result<0,N=1
AND	0100	000:111	000:111	000:111		0	if Result=0,Z=1
							if Result<0,N=1
OR	0101	000:111	000:111	000:111		0	if Result=0,Z=1
							if Result<0,N=1
SHL	0110	000:111			16 bits	1	update carry
							flag
SHR	0111	000:111			16 bits	1	update carry
							flag
IADD	1000	000:111		000:111	16 bits	1	if Result=0,Z=1
							if Result<0,N=1

Table 2: Two Operand Instruction Mapping

0.13 Memory Operations

- 4 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- 16 bits for immediate values.
- 20 bits for effective addresses.
- Total of 8 bits with no immediate values or effective addresses.
- Total of 24 bits with immediate values.
- Total of 28 bits with effective addresses.

Rdst Conditions Operation OpCode EA16|32imm PUSH 1001 000:1110 POP 1010 000:111 0 LDM 1011 000:111 1 16 bits LDD 1100 000:111 20 bits 1 STD 20 bits 1 1101 000:111

Table 3: Memory Instruction Mapping

0.14 Branch and Change Control Operations

- 4 bits (0000) for branching instructions.
- 3 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- Total of 11 bits, padded with 5 0's to fit 16 bits.

Table 4: One Operand Instruction Mapping

Operation	OpCode	Destination	16 32	Conditions
JZ	0000001	000:111	0	
JMP	0000010	000:111	0	
CALL	0000011	000:111	0	
RET	0000100		0	
RTI	0000101		0	

Part IV Control Signals

TODO: Add related control signals for each instruction

Part V Pipeline Stages

0.15 Overview

TODO: Add an overview of how pipelining works in our system

0.16 IF/ID Buffer

TODO: Add buffer components

0.17 ID/EX Buffer

TODO: Add buffer components

0.18 EX/M Buffer

TODO: Add buffer components

0.19 M/WB Buffer

TODO: Add buffer components

0.20 Hazards Detection and Handling

TODO: refactor this section and add more details

0.20.1 Structural Hazards

2 memory units, one for instructions and one for data. Both have the same specs (mentioned below).

Also, to handle register file structural hazard, the write back will be in the first half of the clock cycle and the decode will be in the second half.

0.20.2 Data Hazards

Refer the HDU in 1

Stall

Occurs only at Decode stage, due to load use case.

- Fetch same instruction (don't increment the program counter).
- Latch IF/ID buffer with the same values.
- Freeze Decode stage.
- Clear ID/EX buffer.

Data Forwarding

- EX/MEM buffer -> Execute / Decode.
- ID/EX buffer > Decode.

0.20.3 Control Hazards

- At Fetch stage, always check the branch predictor and calculate the next address accordingly.
- At Decode stage, check whether the OPCode is of a branch operation. If so, pass the address to the program counter and compare the correct address with the address of the counter to decide whether to flush the Fetch stage or not.

Flush

Occurs only at Fetch Stage, due to wrong branch prediction at Decode stage.

- Load new address in the program counter.
- Remove fetched instructions from IF/ID buffer.

Dynamic Branch Prediction

Hash table of some length containing Keys of branch addresses paired with 1-bit for branch prediction.