

5-stage Pipelined Processor Design Report

Team #4

Mohamed Shawky
SEC:2, BN:16

Remonda Talaat
SEC:1, BN:20

Evram Youssef
SEC:1, BN:9

Mahmoud Adas
SEC:2, BN:21

March 30, 2020

Contents

I	Introduction	1
0.1	System Overview	2
0.2	Task Distribution	2
II	Overall System	3
0.3	Overall System Design Schema	4
0.4	Memory Specs	4
0.5	PC Control Unit	5
0.5.1	Inputs	5
0.5.2	Outputs	5
0.5.3	Logic	5
0.6	Dynamic Branch Prediction	5
0.7	Branch Address Unit	6
0.7.1	Inputs	6
0.7.2	Outputs	6
0.7.3	Logic	6
0.8	Register File	6
0.8.1	Registers	6
0.8.2	Inputs	7
0.8.3	Outputs	7
0.8.4	Logic	7
0.9	ALU	7
0.9.1	Inputs	7
0.9.2	Outputs	7
0.9.3	ALU Operations	8
0.9.4	Logic	8

III	Instruction Format	10
0.10	One Operand Operations	11
0.11	Special Operations	11
0.12	Two Operand Operations	11
0.13	Memory Operations	12
0.14	Branch and Change Control Operations	13
IV	Control Signals	14
V	Pipeline Stages	16
0.15	Overview	17
0.16	IF/ID Buffer	17
0.17	ID/EX Buffer	17
0.18	EX/M Buffer	17
0.19	M/WB Buffer	17
VI	Pipeline Hazards and solutions	18
0.20	Hazards Detection and Handling	19
0.20.1	Structural Hazards	19
0.20.2	Data Hazards	19
0.20.3	Control Hazards	19

List of Figures

1	Overall System Design	4
2	Register File Diagram	9

List of Tables

1	One Operand Instruction Mapping	11
2	Two Operand Instruction Mapping	12
3	Memory Instruction Mapping	13
4	One Operand Instruction Mapping	13

Part I

Introduction

0.1 System Overview

This document reports our design work of the 5-stage pipelined processor using Harvard architecture. We discuss the overall system blocks and connections, the functionalities of the different blocks and the hazard solutions.

0.2 Task Distribution

TODO: Task distribution table

Part II

Overall System

0.3 Overall System Design Schema

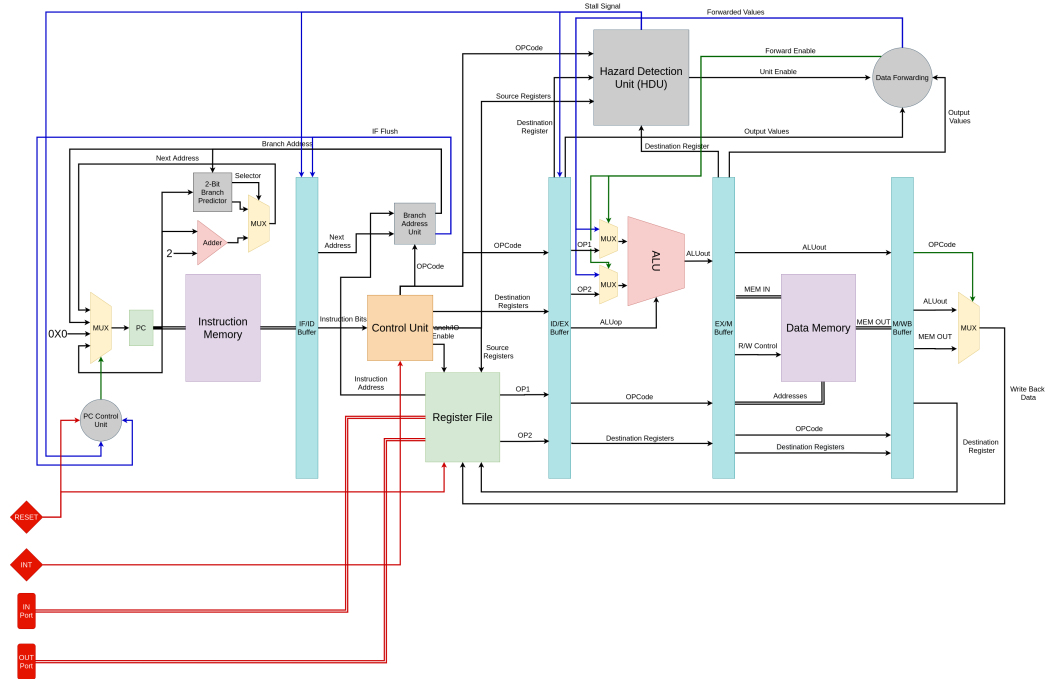


Figure 1: Overall System Design

TODO(1): Add branch predictor design

TODO(2): Add Interrupt handling design

TODO(3): Add stack pointer related instructions design

TODO(4): Add 32-bit fetch detection unit

0.4 Memory Specs

- We have 2 separate memory units, one for instructions and another for data and stack.
- Instruction Memory:
 - $2^{32} \times 16$ bits

- 16-bit bus
- Data Memory:
 - $2^{32} \times 16$ bits
 - 32-bit bus
 - SP starts at $2^{32}-1$

0.5 PC Control Unit

0.5.1 Inputs

- IF Flush (1 bit)
- Stall Signal (1 bit)
- RESET Signal (1 bit)

0.5.2 Outputs

- PC Mux Selectors (2 bits)

0.5.3 Logic

- If IF Flush == 1, Output = 01
- If RESET == 1, Output = 10
- If Stall == 1, Output = 11
- Else, Output = 00

0.6 Dynamic Branch Prediction

TODO: Add branch prediction details in both overall diagram and section

0.7 Branch Address Unit

0.7.1 Inputs

- PC Next Address (32 bits)
- Instruction Address (32 bits)
- OpCode (7 bits)

0.7.2 Outputs

- IF Flush (1 bit)
- Branch Address (32 bits)

0.7.3 Logic

- Check if OpCode is of a branch instruction, if true:
 - Check whether PC Next Address is equal to Instruction Address
 - If true:
 - * IF Flush = 0, Branch Address = Instruction Address
 - If false:
 - * IF Flush = 1, Branch Address = Instruction Address

0.8 Register File

0.8.1 Registers

- 8 general purpose registers
- Stack pointer (SP) register
- Program counter (PC) register

0.8.2 Inputs

- Dest Regs: 2X4 bits (for destination selection)
- SRC Regs: 2X4 bits (for source selection)
- WB values: 2X32 bits (for write back values)
- RESET: 1 bit (for registers clear).
- Branch/IO: 2 bits (to determine whether the operation is IO or branch)
- IN Port: 32 bits (IO input port)

0.8.3 Outputs

- OP1: 32 bits (value of first operand)
- OP2: 32 bits (value of second operand)
- Instruction Address: 32 bits (value of branch address)
- OUT Port: 32 bits (IO output port)

0.8.4 Logic

The register selector acts like a decoder to select the required operation and the register on which the operation performed.

0.9 ALU

0.9.1 Inputs

- ALUop: 4 bits (refer to ALU Operations below)
- Operands: 2X32 bits (2 input operands)

0.9.2 Outputs

- ALUout: 32 bits (operation result)

0.9.3 ALU Operations

- NOP – 0000
- INC – 0001
- DEC – 0010
- ADD – 0011
- SUB – 0100
- AND – 0101
- OR – 0110
- NOT – 0111
- SHL – 1000
- SHR – 1001

0.9.4 Logic

- ALU performs the operation and changes the CCR accordingly.
- The input operands of the ALU are multiplexed between forwarded data and register data, with selectors from data forwarding unit.

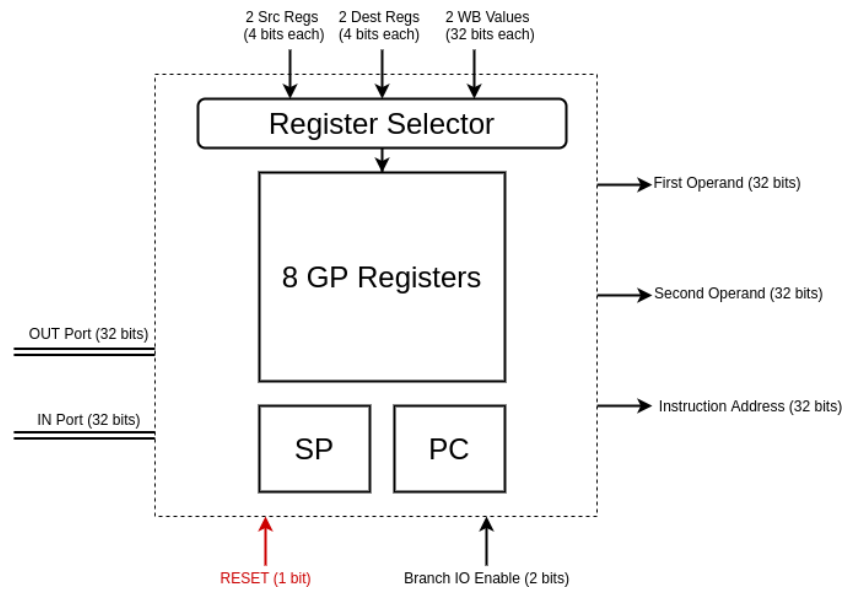


Figure 2: Register File Diagram

Part III

Instruction Format

0.10 One Operand Operations

- 4 bits (1111) for one operand instructions.
- 3 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- Total of 11 bits, padded with 5 0's to fit 16 bits.

Table 1: One Operand Instruction Mapping

Operation	OpCode	Destination	16 32	Conditions
IN	1111000	000:111	0	_____
NOT	1111001	000:111	0	if !Rdst=0,Z=1 if !Rdst<0,N=1
INC	1111010	000:111	0	if Rdst+1=0,Z=1 if Rdst+1<0,N=1
DEC	1111011	000:111	0	if Rdst-1=0,Z=1 if Rdst-1<0,N=1
OUT	1111100	000:111	0	_____

0.11 Special Operations

- 16 0's to represent NOP (0000000000000000).

0.12 Two Operand Operations

- 4 bits to define instruction.
- 3 bits for each of Rsrc1, Rsrc2 and Rdst.
- 1 bit to define the memory slots occupied by the instruction.
- 16 bits for immediate values.
- Total of 14 bits in most cases with some exceptions mentioned below.

Table 2: Two Operand Instruction Mapping

Operation	OpCode	Rsrc1	Rsrc2	Rdst	imm	16 32	Conditions
SWAP	0001	000:111	—	000:111	—	0	—
ADD	0010	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
SUB	0011	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
AND	0100	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
OR	0101	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
SHL	0110	000:111	—	—	16 bits	1	update carry flag
SHR	0111	000:111	—	—	16 bits	1	update carry flag
IADD	1000	000:111	—	000:111	16 bits	1	if Result=0,Z=1 if Result<0,N=1

0.13 Memory Operations

- 4 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- 16 bits for immediate values.
- 20 bits for effective addresses.
- Total of 8 bits with no immediate values or effective addresses.
- Total of 24 bits with immediate values.
- Total of 28 bits with effective addresses.

Table 3: Memory Instruction Mapping

Operation	OpCode	Rdst	imm	EA	16 32	Conditions
PUSH	1001	000:111	—	—	0	_____
POP	1010	000:111	—	—	0	_____
LDM	1011	000:111	16 bits	—	1	_____
LDD	1100	000:111	—	20 bits	1	_____
STD	1101	000:111	—	20 bits	1	_____

0.14 Branch and Change Control Operations

- 4 bits (0000) for branching instructions.
- 3 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- Total of 11 bits, padded with 5 0's to fit 16 bits.

Table 4: One Operand Instruction Mapping

Operation	OpCode	Destination	16 32	Conditions
JZ	0000001	000:111	0	_____
JMP	0000010	000:111	0	_____
CALL	0000011	000:111	0	_____
RET	0000100	—	0	_____
RTI	0000101	—	0	_____

Part IV

Control Signals

TODO: Add related control signals for each instruction

Part V

Pipeline Stages

0.15 Overview

TODO: Add an overview of how pipelining works in our system

0.16 IF/ID Buffer

TODO: Add buffer components

0.17 ID/EX Buffer

TODO: Add buffer components

0.18 EX/M Buffer

TODO: Add buffer components

0.19 M/WB Buffer

TODO: Add buffer components

Part VI

Pipeline Hazards and solutions

0.20 Hazards Detection and Handling

TODO: refactor this section and add more details

0.20.1 Structural Hazards

2 memory units, one for instructions and one for data. Both have the same specs (*mentioned below*).

Also, to handle register file structural hazard, the write back will be in the first half of the clock cycle and the decode will be in the second half.

0.20.2 Data Hazards

Refer the *HDU* in 1

Stall

Occurs only at Decode stage, due to load use case.

- Fetch same instruction (don't increment the program counter).
- Latch IF/ID buffer with the same values.
- Freeze Decode stage.
- Clear ID/EX buffer.

Data Forwarding

- EX/MEM buffer – > Execute / Decode.
- ID/EX buffer – > Decode.

0.20.3 Control Hazards

- At Fetch stage, always check the branch predictor and calculate the next address accordingly.
- At Decode stage, check whether the OPCode is of a branch operation. If so, pass the address to the program counter and compare the correct address with the address of the counter to decide whether to flush the Fetch stage or not.

Flush

Occurs only at Fetch Stage, due to wrong branch prediction at Decode stage.

- Load new address in the program counter.
- Remove fetched instructions from IF/ID buffer.

Dynamic Branch Prediction

Hash table of some length containing Keys of branch addresses paired with 1-bit for branch prediction.