

# 5-stage Pipelined Processor Design Report

Team #4

Mohamed Shawky  
SEC:2, BN:16

Remonda Talaat  
SEC:1, BN:20

Evram Youssef  
SEC:1, BN:9

Mahmoud Adas  
SEC:2, BN:21

April 6, 2020

# Contents

<b>I</b>	<b>Introduction</b>	<b>1</b>
0.1	Abstract . . . . .	2
0.2	Task Distribution . . . . .	2
<b>II</b>	<b>Overall System Design</b>	<b>3</b>
0.3	Overall System Design Schema . . . . .	4
0.4	Memory Specs . . . . .	4
0.5	PC Control Unit . . . . .	5
0.5.1	Inputs . . . . .	5
0.5.2	Outputs . . . . .	5
0.5.3	Logic . . . . .	5
0.6	Dynamic Branch Prediction . . . . .	5
0.6.1	Inputs . . . . .	6
0.6.2	Outputs . . . . .	6
0.6.3	Logic . . . . .	6
0.7	Stack Pointer (SP) Peak Unit . . . . .	6
0.7.1	Inputs . . . . .	6
0.7.2	Outputs . . . . .	6
0.7.3	Logic . . . . .	8
0.8	Branch Address Unit . . . . .	8
0.8.1	Inputs . . . . .	8
0.8.2	Outputs . . . . .	9
0.8.3	Logic . . . . .	9
0.9	Register File . . . . .	9
0.9.1	Registers . . . . .	9
0.9.2	Inputs . . . . .	9
0.9.3	Outputs . . . . .	10

0.9.4	Logic . . . . .	10
0.10	ALU . . . . .	10
0.10.1	Inputs . . . . .	10
0.10.2	Outputs . . . . .	10
0.10.3	ALU Operations . . . . .	11
0.10.4	Logic . . . . .	11
<b>III</b>	<b>Instruction Format</b>	<b>13</b>
0.11	One Operand Operations . . . . .	14
0.12	Special Operations . . . . .	14
0.13	Two Operand Operations . . . . .	14
0.14	Memory Operations . . . . .	15
0.15	Branch and Change Control Operations . . . . .	16
<b>IV</b>	<b>Control Unit (Signals)</b>	<b>17</b>
0.16	Overview . . . . .	18
0.17	Control Signals . . . . .	19
0.17.1	One Operand Instructions . . . . .	20
0.17.2	Two Operand Instructions . . . . .	21
0.17.3	Immediate Operand Instructions . . . . .	21
0.17.4	Data Instructions . . . . .	22
0.18	Stack Instructions . . . . .	23
0.19	Jump Instructions . . . . .	24
0.20	Special Instructions . . . . .	25
<b>V</b>	<b>Pipeline Stages</b>	<b>27</b>
0.21	Overview . . . . .	28
0.21.1	Fetch Stage . . . . .	28
0.21.2	Decode Stage . . . . .	28
0.21.3	Execute Stage . . . . .	28
0.21.4	Memory Stage . . . . .	29
0.21.5	Write-Back Stage . . . . .	29
0.22	IF/ID Buffer . . . . .	29
0.22.1	Registers . . . . .	29
0.22.2	Control Signals . . . . .	29

0.23	ID/EX Buffer . . . . .	29
0.23.1	Registers . . . . .	29
0.23.2	Control Signals . . . . .	30
0.24	EX/M Buffer . . . . .	30
0.24.1	Registers . . . . .	30
0.24.2	Control Signals . . . . .	30
0.25	M/WB Buffer . . . . .	30
0.25.1	Registers . . . . .	30
<b>VI</b>	<b>Pipeline Hazards and solutions</b>	<b>32</b>
0.26	Structural Hazards . . . . .	33
0.26.1	Detection . . . . .	33
0.26.2	Handling . . . . .	33
0.27	Data Hazards . . . . .	33
0.27.1	Detection . . . . .	33
0.27.2	Handling . . . . .	33
0.28	Control Hazards . . . . .	34
0.28.1	Detection . . . . .	34
0.28.2	Handling . . . . .	34

# List of Figures

1	Overall System Design . . . . .	4
2	Branch Prediction Unit Diagram . . . . .	7
3	Stack Pointer (SP) Peak Unit Diagram . . . . .	7
4	Branch Address Unit Diagram . . . . .	8
5	Register File Diagram . . . . .	12
6	Hazard Detection Unit Diagram . . . . .	36

# List of Tables

1	Task Distribution . . . . .	2
2	One Operand Instruction Mapping . . . . .	14
3	Two Operand Instruction Mapping . . . . .	15
4	Memory Instruction Mapping . . . . .	16
5	One Operand Instruction Mapping . . . . .	16
6	One Operand Instruction Control Signals Part I . . . . .	20
7	One Operand Instruction Control Signals Part II . . . . .	20
8	Two Operands Instruction Control Signals Part I . . . . .	21
9	Two Operands Instruction Control Signals Part II . . . . .	21
10	Immediate Operand Instruction Control Signals Part I . . . . .	22
11	Immediate Operand Instruction Control Signals Part II . . . . .	22
12	Data Instruction Control Signals Part I . . . . .	23
13	Data Instruction Control Signals Part II . . . . .	23
14	Stack Instruction Control Signals Part I . . . . .	24
15	Stacks Instruction Control Signals Part II . . . . .	24
16	Jumpers Instruction Control Signals Part I . . . . .	25
17	Jumpers Instruction Control Signals Part II . . . . .	25
18	Specials Instruction Control Signals Part I . . . . .	25
19	Specials Instruction Control Signals Part II . . . . .	25

# Part I

## Introduction

## 0.1 Abstract

This report describes our design work of the 5-stage pipelined processor, that follows Harvard architecture.

This report contains:

- the overall system blocks and connections.
- the functionalities of the different blocks.
- the hazard solutions.

## 0.2 Task Distribution

Table 1 contains the task distribution.

Table 1: Task Distribution

Team Member	Tasks
Mohamed Shawky	<ul style="list-style-type: none"> <li>– Overall system design.</li> <li>– Hazard detection and handling.</li> <li>– Document typing and formatting.</li> </ul>
Remonda Talaat	<ul style="list-style-type: none"> <li>– Instruction format.</li> <li>– Interrupt Handling.</li> <li>– Overall system design.</li> </ul>
Evram Youssef	<ul style="list-style-type: none"> <li>– Control unit and its signals.</li> <li>– Low level block design.</li> <li>– Pipeline buffers.</li> </ul>
Mahmoud Adas	<ul style="list-style-type: none"> <li>– Low level block design.</li> <li>– Pipeline buffers.</li> <li>– Document typing and formatting.</li> </ul>



# **Part II**

## **Overall System Design**

### 0.3 Overall System Design Schema

Figure 1 shows the overall system design in detail. Each unit is described in details in its section.

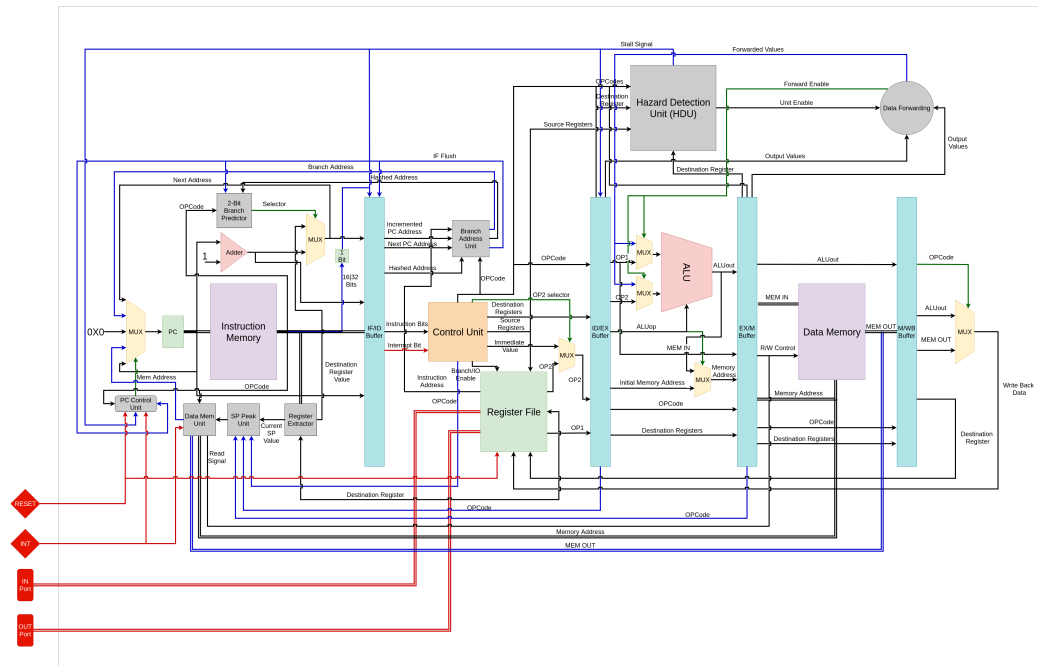


Figure 1: Overall System Design

## 0.4 Memory Specs

Because the design follows Harvard architecture, it uses 2 separate memory units, one for instructions and another one for both the data and stack.

- Instructions Memory:
  - $2^{32} \times 16$  bits
  - 16-bit bus
- Data Memory:

- $2^{32} \times 16$  bits
- 32-bit bus
- SP starts at  $2^{32}-1$

## 0.5 PC Control Unit

### 0.5.1 Inputs

- IF Flush (1 bit)
- Stall Signal (1 bit)
- RESET Signal (1 bit)
- Interrupt Signal (1 bit)
- Current OPCode (7 bits)

### 0.5.2 Outputs

- PC Mux Selectors (3 bits)

### 0.5.3 Logic

- If IF Flush == 1, Output = 001
- If RESET == 1, Output = 010
- If Stall == 1, Output = 011
- If Interrupt == 1 || OPCode == RET/RTI, Output = 100
- Else, Output = 000

## 0.6 Dynamic Branch Prediction

Figure 2 shows the branch prediction unit.

### 0.6.1 Inputs

- Hashed Address (4 bits)
- Update Bit (1 bit): *Taken or Not* to update FSM
- OPcode (4 bits)

### 0.6.2 Outputs

- Taken (1 bit): predict whether the branch taken or not

### 0.6.3 Logic

- Updates the FSM corresponding to the hashed address.
- Checks whether the OPCode is of a conditional branch instruction.
- Outputs the prediction bit (*Taken or Not*) accordingly.

## 0.7 Stack Pointer (SP) Peak Unit

Figure 3 shows the stack pointer unit.

### 0.7.1 Inputs

- Current SP (32 bits)
- Prev OPCODEs (3X7 bits)

### 0.7.2 Outputs

- Expected SP (32 bits): stack pointer to read from after eliminating hazards

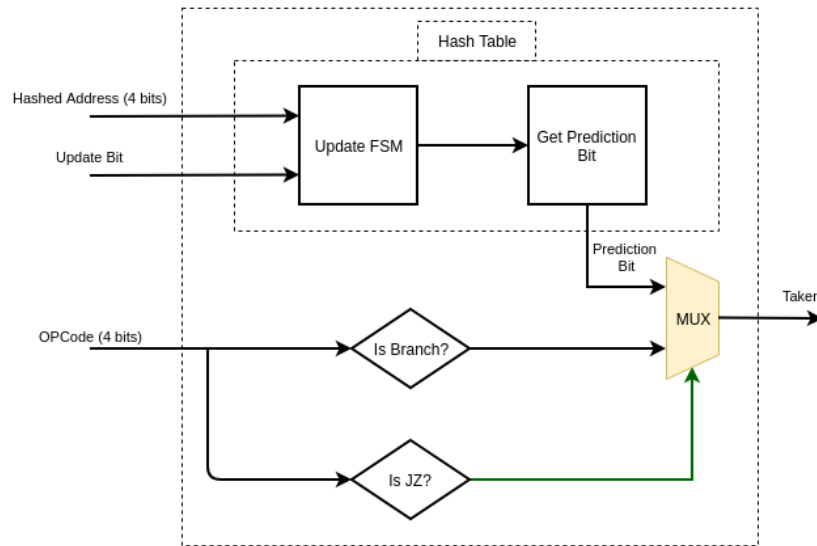


Figure 2: Branch Prediction Unit Diagram

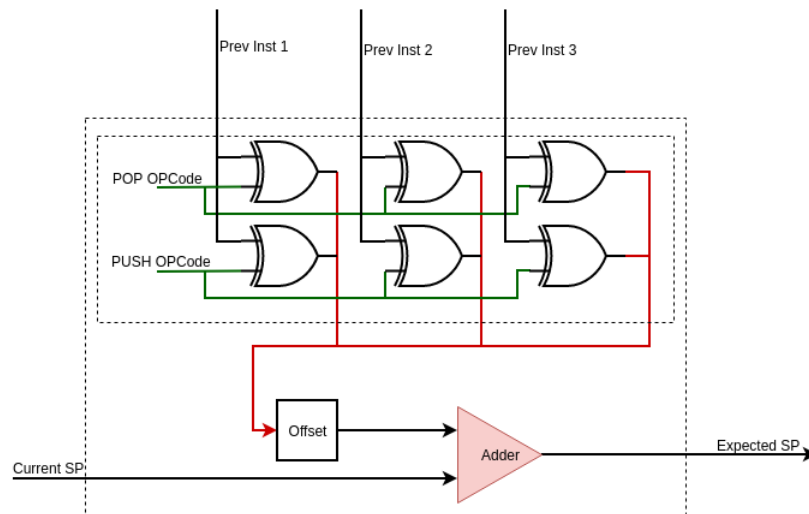


Figure 3: Stack Pointer (SP) Peak Unit Diagram

### 0.7.3 Logic

This unit peaks the value of the stack pointer on returning from a subroutine or an interrupt, in order to calculate the correct value of the address from which the original program counter read from memory. It checks for *POP/PUSH* instructions and use the count to update the address.

**NOTE:** In case we didn't use this unit, we will stall the pipe for three consecutive cycles to eliminate possible hazards.

## 0.8 Branch Address Unit

Figure 4 shows the branch address unit.

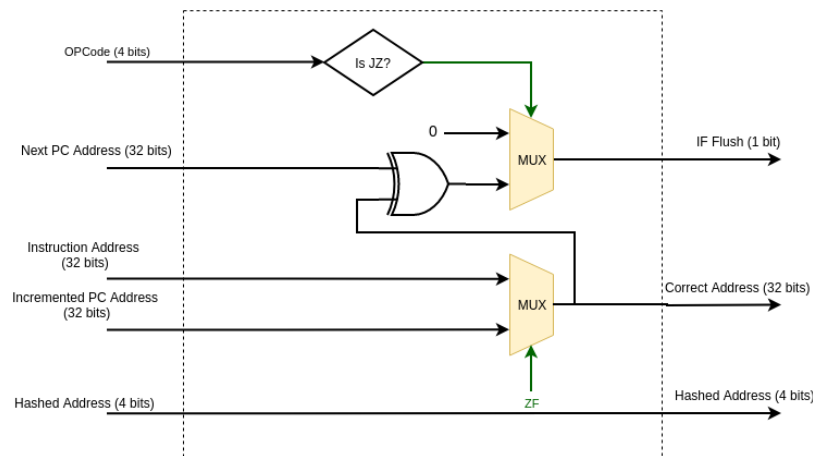


Figure 4: Branch Address Unit Diagram

### 0.8.1 Inputs

- Next PC Address (32 bits)
- Instruction Address (32 bits)
- Incremented PC Address (32 bits)
- Hashed Address (4 bits)

- OpCode (4 bits)

### 0.8.2 Outputs

- IF Flush (1 bit)
- Branch Address (32 bits)
- Hashed Address (4 bits)

### 0.8.3 Logic

- Check if OpCode is of a conditional branch instruction, if true:
  - Check whether PC Next Address is equal to Instruction Address
  - If true:
    - \* IF Flush = 0, Branch Address = Instruction Address
  - If false:
    - \* IF Flush = 1, Branch Address = Instruction Address

## 0.9 Register File

Figure 5 shows the register file.

### 0.9.1 Registers

- 8 general purpose registers
- Stack pointer (SP) register
- Program counter (PC) register

### 0.9.2 Inputs

- Dest Regs: 2X4 bits (for destination selection)
- SRC Regs: 2X4 bits (for source selection)

- Fetch Reg: 4 bits (for fetch branch register selection)
- WB values: 2X32 bits (for write back values)
- RESET: 1 bit (for registers clear).
- Branch/IO: 2 bits (to determine whether the operation is IO or branch)
- IN Port: 32 bits (IO input port)

### 0.9.3 Outputs

- OP1: 32 bits (value of first operand)
- OP2: 32 bits (value of second operand)
- Fetch Value: 32 bits (value of branch address required by fetch)
- Instruction Address: 32 bits (value of branch address)
- OUT Port: 32 bits (IO output port)

### 0.9.4 Logic

The register selector acts like a decoder to select the required operation and the register on which the operation performed.

## 0.10 ALU

### 0.10.1 Inputs

- ALUop: 4 bits (refer to ALU Operations below)
- Operands: 2X32 bits (2 input operands)

### 0.10.2 Outputs

- ALUout: 32 bits (operation result)



### 0.10.3 ALU Operations

- 0000 – NOP – (no operation)
- 0001 – INC – (first operand + 1)
- 0010 – DEC – (first operand - 1)
- 0011 – ADD – (first operand + second operand)
- 0100 – SUB – (first operand - second operand)
- 0101 – AND – (first operand && second operand)
- 0110 – OR – (first operand || second operand)
- 0111 – NOT – (!first operand)
- 1000 – SHL – (shift first operand to the left)
- 1001 – SHR – (shift first operand to the right)
- 1010 – INC2 – (first operand + 2)
- 1011 – DEC2 – (first operand - 2)
- 1100 – INC4 – (first operand + 4)
- 1101 – DEC4 – (first operand - 4)

### 0.10.4 Logic

- ALU performs the operation and changes the CCR accordingly.
- The input operands of the ALU are multiplexed between forwarded data and register data, with selectors from data forwarding unit.

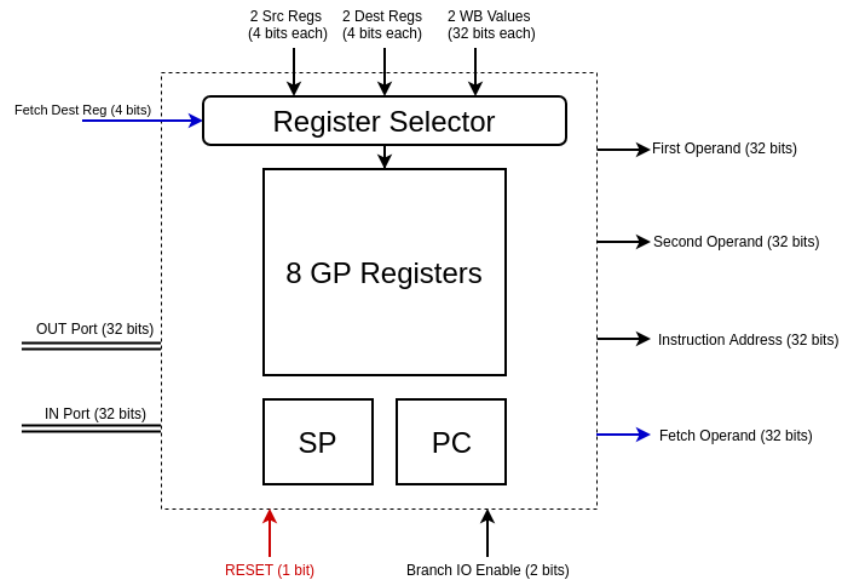


Figure 5: Register File Diagram

# **Part III**

## **Instruction Format**

## 0.11 One Operand Operations

- 4 bits (1111) for one operand instructions.
- 3 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- Total of 11 bits, padded with 5 0's to fit 16 bits.

Table 2: One Operand Instruction Mapping

Operation	OpCode	Destination	16 32	Conditions
IN	1111000	000:111	0	_____
NOT	1111001	000:111	0	if !Rdst=0,Z=1 if !Rdst<0,N=1
INC	1111010	000:111	0	if Rdst+1=0,Z=1 if Rdst+1<0,N=1
DEC	1111011	000:111	0	if Rdst-1=0,Z=1 if Rdst-1<0,N=1
OUT	1111100	000:111	0	_____

## 0.12 Special Operations

- 16 0's to represent NOP (0000000000000000).

## 0.13 Two Operand Operations

- 4 bits to define instruction.
- 3 bits for each of Rsrc1, Rsrc2 and Rdst.
- 1 bit to define the memory slots occupied by the instruction.
- 16 bits for immediate values.
- Total of 14 bits in most cases with some exceptions mentioned below.

Table 3: Two Operand Instruction Mapping

Operation	OpCode	Rsrc1	Rsrc2	Rdst	imm	16 32	Conditions
SWAP	0001	000:111	—	000:111	—	0	—
ADD	0010	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
SUB	0011	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
AND	0100	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
OR	0101	000:111	000:111	000:111	—	0	if Result=0,Z=1 if Result<0,N=1
SHL	0110	000:111	—	—	16 bits	1	update carry flag
SHR	0111	000:111	—	—	16 bits	1	update carry flag
IADD	1000	000:111	—	000:111	16 bits	1	if Result=0,Z=1 if Result<0,N=1

## 0.14 Memory Operations

- 4 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- 16 bits for immediate values.
- 20 bits for effective addresses.
- Total of 8 bits with no immediate values or effective addresses.
- Total of 24 bits with immediate values.
- Total of 28 bits with effective addresses.

Table 4: Memory Instruction Mapping

Operation	OpCode	Rdst	imm	EA	16 32	Conditions
PUSH	1001	000:111	—	—	0	—————
POP	1010	000:111	—	—	0	—————
LDM	1011	000:111	16 bits	—	1	—————
LDD	1100	000:111	—	20 bits	1	—————
STD	1101	000:111	—	20 bits	1	—————

## 0.15 Branch and Change Control Operations

- 4 bits (0000) for branching instructions.
- 3 bits to define instruction.
- 3 bits for destination register.
- 1 bit to define the memory slots occupied by the instruction.
- Total of 11 bits, padded with 5 0's to fit 16 bits.

Table 5: One Operand Instruction Mapping

Operation	OpCode	Destination	16 32	Conditions
JZ	0000001	000:111	0	—————
JMP	0000010	000:111	0	—————
CALL	0000011	000:111	0	—————
RET	0000100	—	0	—————
RTI	0000101	—	0	—————

# **Part IV**

## **Control Unit (Signals)**

## 0.16 Overview

Control unit is responsible for generating the control signals that are used to activate several operations throughout the pipeline. Also, it's responsible for the extraction of specific information from instruction bits.

- It communicates with:
  - IF/ID buffer: for reading the instruction bits.
  - ID/EX buffer: for writing the appropriate registers, ALUop and signals.
  - Register file: for selecting the registers needed to be read (Rsrc1 and Rsrc2).
  - Hazards units (HDU and Branch Address Unit): for sending enables and needed signals.
- Unit Interface:
  - Inputs:
    - \* Instruction Bits (32 bits)
    - \* Interrupt bit (1 bit)
  - Outputs:
    - \* Rsrc2\_val (32 bits) for immediate values or effective addresses
    - \* Rsrc1\_sel (4 bits)
    - \* Rsrc2\_sel (4 bits)
    - \* Rdst1\_sel (4 bits)
    - \* Rdst2\_sel (4 bits) used only in case of swap
    - \* Branch/IO Enable (2 bits)
    - \* OP2\_sel (1 bit)
    - \* SP Enable (1 bit)
    - \* OpCode (7 bits)
    - \* Branch Enable (1 bit)
    - \* ALUop (4 bits)
    - \* R/W Control Signal (2 bits)
- Interpretation:



- **Rsrc2\_val (32 bits):** occupies a single place in the ID/EX buffer. However, it's used in many different ways. It can be used as a register value extracted from register file. It can be used as an immediate value extracted from IF/ID buffer. Also, it can hold the stack pointer address, as well as the effective address (EA) sent to the memory for reading or writing.
- **Rdst2 (4 bits):** only used when dealing with a SWAP instruction, thus we need Op1 and Op2 and their new selectors.
- **OP2\_sel (1 bit):** determines the value of Rsrc2 register in ID/EX buffer, whether it's immediate or register value.
- **Branch/IO Enable (2 bits):** informs the register file what operation of these are we executing (No/In/Out/Branch), however *Branch Enable* (1 bit) interacts with the Branch Address Unit, informing it what type of OpCode are we dealing with (branching or not).

## 0.17 Control Signals

In this section, instructions are divided into seven types based on the signals produced:

- One Operand (not,inc,dec,out,in).
- Two Operands (add,sub,and,or).
- Immediate Operand (iadd,shl,shr,ldm).
- Data (ldd,std).
- Stack (push,pop,call,ret,rti).
- Jump (jz, jmp).
- Special (nop,swap,reset,int).

### 0.17.1 One Operand Instructions

- IB[31:0] are the instruction bits.
- Inserting (1111) to Rsrc/Rdst selectors informs the register file not to output any register values.
- 'x' indicates don't care.
- 0000 at the ALUop indicates no operation.
- Rsrc1\_sel is the same as Rdst1\_sel.

Table 6: One Operand Instruction Control Signals Part I

Instruction	OPCode	ALUop	Rsrc1 selector	Rsrc2 selector	Rdst1 selector	Rsrc2 value
NOT	IB[31:25]	0111	0 and IB[24:22]	1111	0 and IB[24:22]	x
INC	IB[31:25]	0001	0 and IB[24:22]	1111	0 and IB[24:22]	x
DEC	IB[31:25]	0010	0 and IB[24:22]	1111	0 and IB[24:22]	x
OUT	IB[31:25]	0000	0 and IB[24:22]	1111	0 and IB[24:22]	x
IN	IB[31:25]	0000	0 and IB[24:22]	1111	0 and IB[24:22]	x

Table 7: One Operand Instruction Control Signals Part II

Instruction	OP2 selector	Rdst2 (swap)	Branch /IO Enable	SP Enable	Branch Enable	R/W Control Signal
NOT	x	1111	00	0	0	00
INC	x	1111	00	0	0	00
DEC	x	1111	00	0	0	00
OUT	x	1111	01	0	0	00
IN	x	1111	10	0	0	00

### 0.17.2 Two Operand Instructions

- OP2\_sel: 0 the register value and 1 the imm/ea value.

Table 8: Two Operands Instruction Control Signals Part I

Instruction	OPCode	ALUOp	Rsrc1 selector	Rsrc2 selector	Rdst1 selector	Rsrc2 value
ADD	IB[31:25]	0011	0 and IB[27:25]	0 and IB[24:22]	0 and IB[21:19]	x
SUB	IB[31:25]	0100	0 and IB[27:25]	0 and IB[24:22]	0 and IB[21:19]	x
AND	IB[31:25]	0101	0 and IB[27:25]	0 and IB[24:22]	0 and IB[21:19]	x
OR	IB[31:25]	0110	0 and IB[27:25]	0 and IB[24:22]	0 and IB[21:19]	x

Table 9: Two Operands Instruction Control Signals Part II

Instruction	OP2 se- lector	Rdst2 (swap)	Branch /IO Enable	SP En- able	Branch Enable	R/W Control Signal
ADD	0	1111	00	0	0	00
SUB	0	1111	00	0	0	00
AND	0	1111	00	0	0	00
OR	0	1111	00	0	0	00

### 0.17.3 Immediate Operand Instructions

- Rsrc1\_sel is the same as Rdst1\_sel, in SHL and SHR cases. However, in IADD case, it's a different register and in LDM case, there's no need for Rsrc, it's just a destination.
- In IADD case, Rsrc != Rdst.
- In LDM case, there's no Rsrc, it's Rdst.
- Rsrc2\_val is the immediate value extracted from the IF/ID buffer.

- R/W memory (11) is write and (10) is read.
- Sign extend unit is used to adjust the (16 bits) immediate value to (32 bits).
- SE: sign extend enable (0/1).

Table 10: Immediate Operand Instruction Control Signals Part I

Instruction	OPCode	ALUOp	Rsrc1 selector	Rsrc2 selector	Rdst1 selector	Rsrc2 value
IADD	IB[31:25]	0011	0 and IB[27:25]	1111	0 and IB[24:22]	0XSE and IB[15:0]
SHL	IB[31:25]	1000	0 and IB[27:25]	1111	0 and IB[27:25]	0XSE and IB[15:0]
SHR	IB[31:25]	1001	0 and IB[27:25]	1111	0 and IB[27:25]	0XSE and IB[15:0]
LDM	IB[31:25]	0000	1111	1111	0 and IB[27:25]	0XSE and IB[15:0]

Table 11: Immediate Operand Instruction Control Signals Part II

Instruction	OP2 se- lector	Rdst2 (swap)	Branch /IO Enable	SP En- able	Branch Enable	R/W Control Signal
IADD	1	1111	00	0	0	00
SHL	1	1111	00	0	0	00
SHR	1	1111	00	0	0	00
LDM	1	1111	00	0	0	11

### 0.17.4 Data Instructions

Note that:

- Effective address does not need a sign extend, that's why it's always zero extended with only 12 bits.
- OP2\_sel is 1 to pass the EA.
- R/W memory (11) is write and (10) is read.

Table 12: Data Instruction Control Signals Part I

Instruction	OPCode	ALUOp	Rsrc1 selector	Rsrc2 selector	Rdst1 selector	Rsrc2 val
LDD	IB[31:25]	0000	0 and IB[27:25]	1111	1111	0x000 and IB[19:0]
STD	IB[31:25]	0000	1111	1111	0 and IB[27:25]	0x000 and IB[19:0]

Table 13: Data Instruction Control Signals Part II

Instruction	OP2 se- lector	Rdst2 (swap)	Branch /IO Enable	SP En- able	Branch Enable	R/W Control Signal
LDD	1	1111	00	0	0	10
STD	1	1111	00	0	0	11

## 0.18 Stack Instructions

- Rsrc2\_val is the stack pointer, as it's the address of the operation.
- ALUOp's Inc2 and Dec2 are used to manipulate the stack pointer, thus the output of the ALU will be the new stack pointer.
- In case of Call, Rsrc1\_sel is none, as no register is used. It is the PC pushed at the memory.
- In case of Call, Rdst1\_sel, is the register holding the new address.

- In case of Ret and Rti, no registers are affected, as the PC is updated at the fetch stage.
- R/W memory (11) is write and (10) is read.

Table 14: Stack Instruction Control Signals Part I

Instruction	OPCode	ALUOp	Rsrc1 selector	Rsrc2 selector	Rdst1 selector	Rsrc2 val
PUSH	IB[31:25]	1011	0 and IB[27:25]	1111	1111	SP(32 bits)
POP	IB[31:25]	1010	1111	1111	0 and IB[27:25]	SP(32 bits)
CALL	IB[31:25]	1011	1111	1111	0 and IB[27:25]	SP(32 bits)
RET	IB[31:25]	1010	1111	1111	1111	SP(32 bits)
RTI	IB[31:25]	1100	1111	1111	1111	SP(32 bits)

Table 15: Stacks Instruction Control Signals Part II

Instruction	OP2 se- lector	Rdst2 (swap)	Branch /IO Enable	SP En- able	Branch Enable (JZ)	R/W Control Signal
PUSH	1	1111	00	1	0	11
POP	1	1111	00	0	0	10
CALL	1	1111	00	0	0	11
RET	1	1111	00	0	0	10
RTI	1	1111	00	0	0	10

## 0.19 Jump Instructions

- Rsrc1\_sel is the address we are jumping to, that's why we need to verify that our prediction at the JZ case is correct.
- Branch/IO Enable is (11) as it is a branching instruction.

- Branch enable (1) to detect if the JZ operated correctly.

Table 16: Jumpers Instruction Control Signals Part I

Instruction	OPCode	ALUOp	Rsrc1 selector	Rsrc2 selector	Rdst1 selector	Rsrc2 val
JMP	IB[31:25]	0000	1111	1111	1111	x
JZ	IB[31:25]	0000	0 and IB[27:25]	1111	1111	x

Table 17: Jumpers Instruction Control Signals Part II

Instruction	OP2 se- lector	Rdst2 (swap)	Branch /IO Enable	SP En- able	Branch Enable (JZ)	R/W Control Signal
JMP	x	1111	11	0	0	00
JZ	x	1111	11	0	1	00

## 0.20 Special Instructions

There's no interrupt instruction, but there's a bit called Interrupt, sent to the Control Unit as an input to indicate an interrupt signal was triggered.

Table 18: Specials Instruction Control Signals Part I

Instruction	OPCode	ALUOp	Rsrc1 selector	Rsrc2 selector	Rdst1 selector	Rsrc2 val
NOP	IB[31:25]	0000	1111	1111	1111	x
SWAP	IB[31:25]	0000	0 and IB[27:25]	0 and IB[24:22]	0 and IB[24:22]	x
Reset	IB[31:25]	0000	1111	1111	1111	x
Int	IB[31:25]	0000	1111	1111	1111	x

Table 19: Specials Instruction Control Signals Part II

Instruction	OP2 selector	Rdst2 (swap)	Branch /IO Enable	SP Enable	Branch Enable (JZ)	R/W Control Signals
NOP	x	1111	00	0	0	00
SWAP	0	0 and IB[27:25]	00	0	0	11
Reset	x	1111	00	0	0	00
Int	x	1111	00	0	0	00



# Part V

## Pipeline Stages

## 0.21 Overview

This section discusses the 5 stages of our system and their functionalities.

### 0.21.1 Fetch Stage

- Responsible for fetching the next instruction.
- Can take two cycles in case of 32-bit instructions.
- Contains a branch prediction unit to determine the next address to be fetched in case of branching.
- Outputs the instruction bits into IF/ID Buffer.
- The current instruction is fetched at the first half of cycle, then the next PC value calculations are done in the second half.

### 0.21.2 Decode Stage

- Responsible for decoding the instruction bits into control signals.
- Outputs the corresponding signals to ID/EX Buffer.
- Contains register file to output operand values and register-related operations.
- Determines the correct branch address in case of branching instructions by using Branch Address Unit.
- The control unit deduces the corresponding signals in the first half of cycle, then the register operations and branch address calculation are done in the second half of cycle.

### 0.21.3 Execute Stage

- Responsible for ALU operations.
- Determines the correct ALU output and pass it with other signals to EX/M Buffer.
- The ALU operations and CCR update are done in the first half of cycle.

### 0.21.4 Memory Stage

- Responsible for Data Memory IO.
- Memory read/write is done in the first half of cycle.

### 0.21.5 Write-Back Stage

- Responsible for passing correct output values to the destination registers.
- Write back is done in the first half of cycle.

## 0.22 IF/ID Buffer

### 0.22.1 Registers

- Instruction Register (32 bits)
- Next Address Register (32 bits)
- Incremented PC Register (32 bits)
- Hashed Address Register (4 bits)
- Interrupt Register (1 bit)

### 0.22.2 Control Signals

- Flush: clear buffer (1 bit)
- Stall: freeze buffer (1 bit)

## 0.23 ID/EX Buffer

### 0.23.1 Registers

- Operand Registers ( $2 \times 32$  bits)
- Destination Register (4 bits)

- OpCode Register (7 bits)
- R/W Register (2 bits)

### **0.23.2 Control Signals**

- Stall (IN): freeze buffer (1 bit)
- Destination Register (OUT) (4 bits)
- Output Values (OUT) (32 bits)

## **0.24 EX/M Buffer**

### **0.24.1 Registers**

- ALUout Register (32 bits)
- MEM IN Register (32 bits)
- Opcode Register (7 bits)
- Destination Register (4 bits)
- R/W Register (2 bits)

### **0.24.2 Control Signals**

- Destination Register (OUT) (4 bits)
- Output Values (OUT) (32 bits)

## **0.25 M/WB Buffer**

### **0.25.1 Registers**

- ALUout Register (32 bits)
- MEM OUT (32 bits)

- OpCode (7 bits)
- Destination Register (4 bits)

## **Part VI**

# **Pipeline Hazards and solutions**

## 0.26 Structural Hazards

### 0.26.1 Detection

The structural hazard occurs in data memory and register file.

### 0.26.2 Handling

The structural hazard in data memory is solved by using 2 memory units, one for instructions and one for data. Both have the same specs (*previously mentioned*).

However structural hazard in register file is handled by forcing the write back to happen in the first half of the clock cycle and the decode to happen in the second half.

## 0.27 Data Hazards

### 0.27.1 Detection

#### Hazard Detection Unit (HDU)

Figure 6 shows the hazard detection unit.

HDU consists of 3 parts:

- **OPCode Checker:** checks the opcode of the current instruction to check whether it will cause data hazard or not, then activates the Register Comparator accordingly. Also, it checks for *load-use case*, in order to activate the stall signal.
- **Register Comparator:** compares the decode source registers with the destination registers of the execute and memory stages.
- **Output Unit:** outputs stall signal in case of load and pop instructions and data forward unit enable in case of other data hazards.

### 0.27.2 Handling

#### Stall

Occurs only at Fetch and Decode stage, due to load(pop) use case.

- Fetch same instruction (don't increment the program counter).
- Latch IF/ID buffer with the same values.
- Freeze Decode stage.
- Clear ID/EX buffer.

### Data Forwarding

- EX/MEM buffer – > Execute / Decode.
- ID/EX buffer – > Decode.

## 0.28 Control Hazards

### 0.28.1 Detection

The branch address calculation occurs in the Decode stage. So, the hazard might affect only the Fetch stage, which will be flushed in case of wrong address prediction.

### 0.28.2 Handling

- At Fetch stage, always check the branch predictor and calculate the next address accordingly.
- At Decode stage, we have a *Branch Address Unit* that checks whether the OPCode is of a branch operation. If so, it passes the address to the program counter and compares the correct address with the address of the counter to decide whether to flush the Fetch stage or not.

### Flush

Occurs only at Fetch Stage, due to wrong branch prediction at Decode stage.

- Load new address in the program counter.
- Remove fetched instructions from IF/ID buffer.



**Dynamic Branch Prediction**

We use 2-bit branch predictor, which is a hash table of *Finite State Machines* (FSMs) to predict whether the branch will be taken (1) or not (0) at each individual branch address.

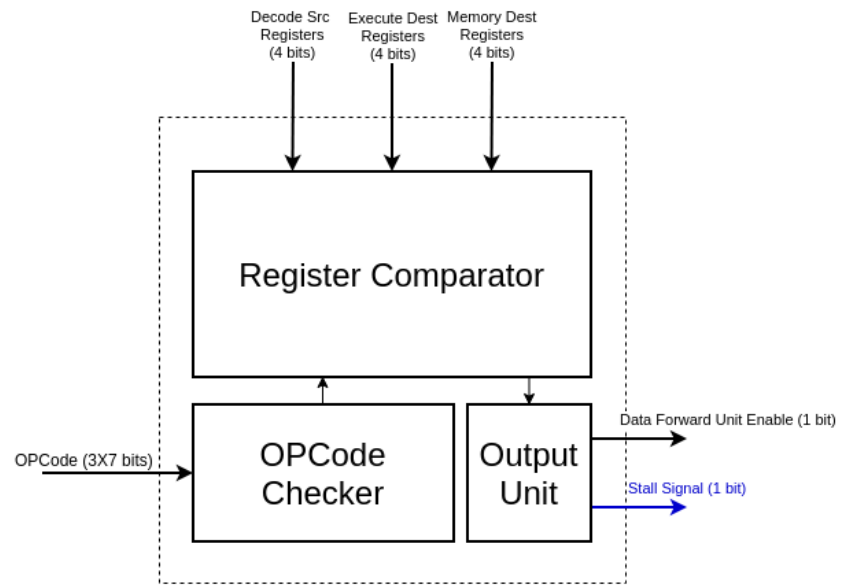


Figure 6: Hazard Detection Unit Diagram